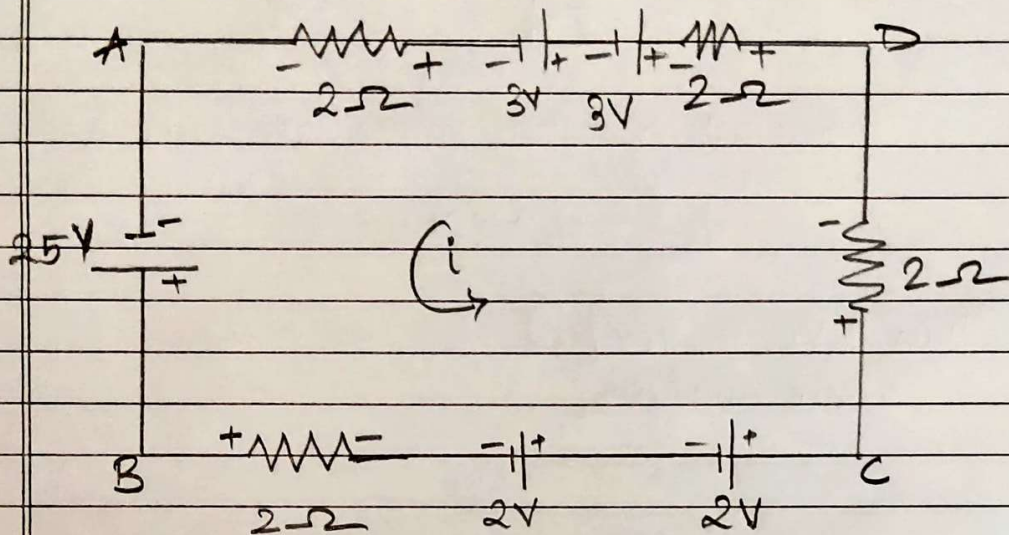


- Q1) Apply KVL and find voltage across the given circuit resistors.



Applying KVL to loop ABCDA.

Assume a current 'i' flows in anticlockwise direction.

$$\therefore V_2 + V_2 + V_2 + V_2 = 2 + 2 - 3 - 3 + 25$$

$$4V_2 = 23$$

$$4 \times 2 \times I_2 = 23$$

$$\boxed{I = 2.875 \text{ A}}$$

* Added the voltages as there is same current flowing through same value of resistors.

$$R_{\text{net}} = 8 \Omega$$

$$V_{\text{net}} = I R_{\text{net}}$$

$$= 2.875 \times 8 = 23$$

Applying voltage division to find voltage across each resistor.

$$V_2 = \frac{23 \times 2}{8} \quad (\text{This is same as applying})$$

ohm's law $V=IR$

$V_2 = 5.75 \text{ V}$

Since all resistor values are same and currents too

$$V_{\text{all}} = 5.75 \text{ V}$$

Thus KVL is verified from from the above analysis.

