

EXPERIMENT:

No. 6

Verification of Norton's


Page No.

Date

Theorem.

Q. Find the Norton's Equivalent for the below circuit.  
about 1.5  $\Omega$  resistor

Circuit:-

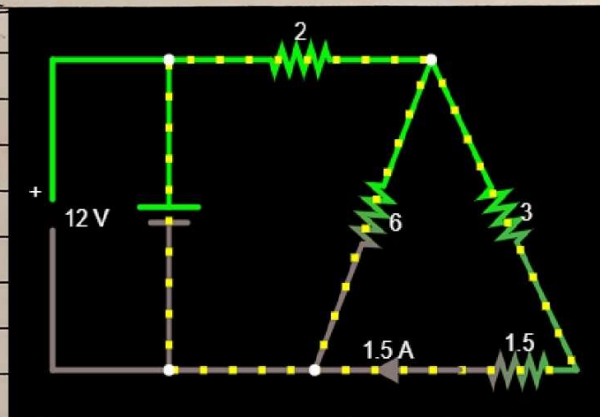

Now removing 1.5  $\Omega$  resistor and finding  
Norton's current ~~also~~ as shown.  
First finding  $R_{net}$

$$R_{net} = 2 + \frac{3 \times 6}{9} = 4 \Omega$$

$$V = IR$$

$$12 = (I) \times 4$$


$$I = 3A$$


Applying current division,

$$I_3 = \frac{6 \times 3}{6 + 3} = \underline{2A}$$

$$I_3 = I_{N0} = \underline{2A}$$

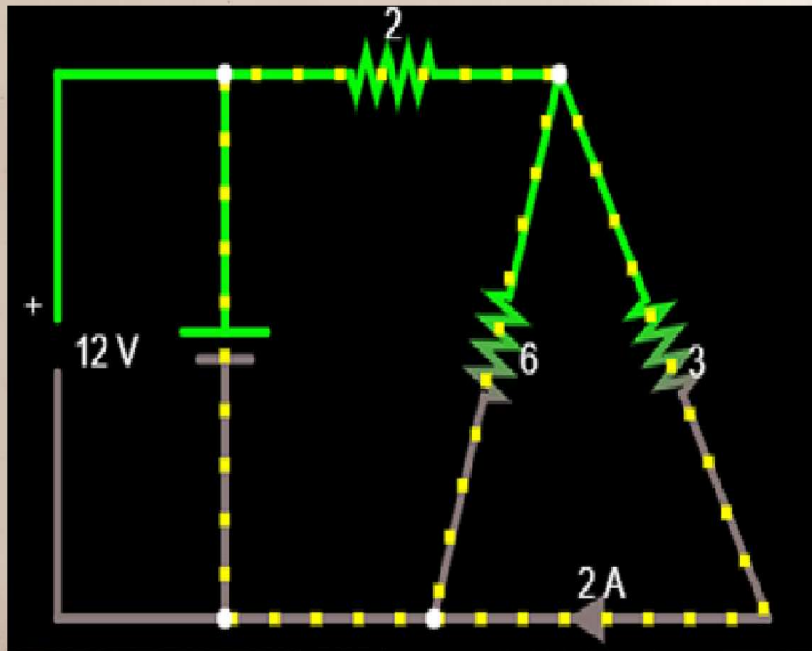Which is quite evident as seen in the simulation



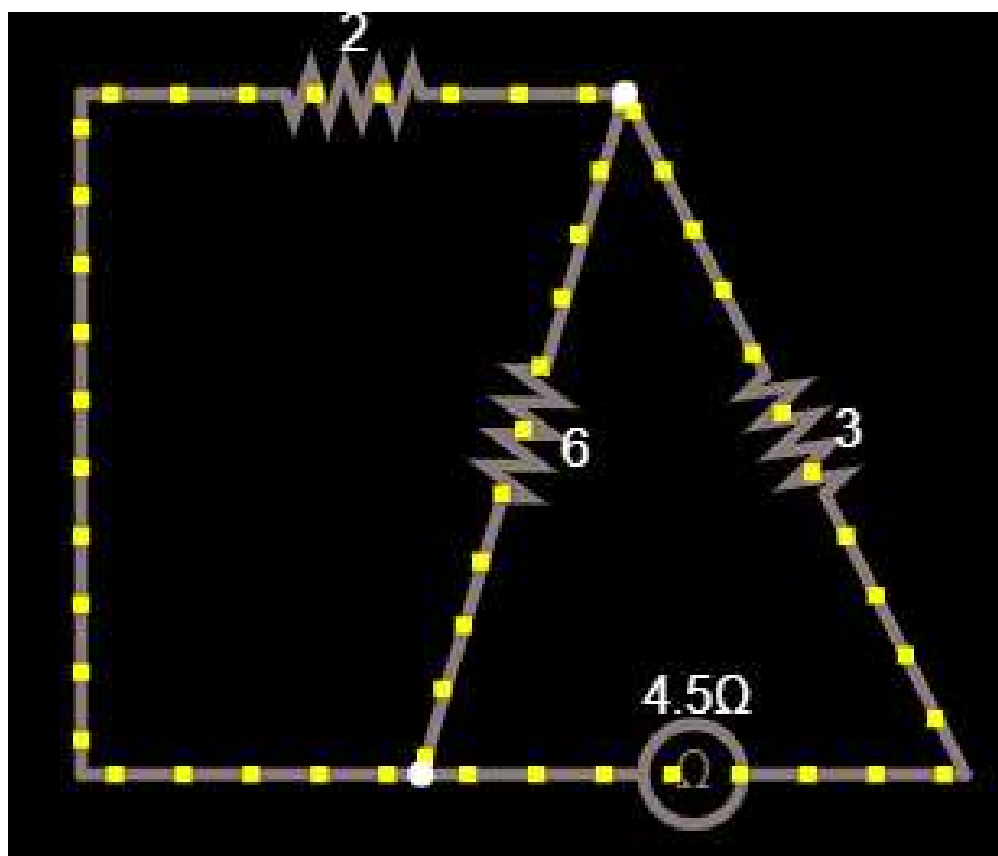

EXPERIMENT:

No.

Page No.

Date


Computing  $R_{No}$ :-

Short the voltage source.

$$R_{No} = 3 + \frac{2 \times 6}{8} = 3 + 1.5 = 4.5 \Omega$$

Thus  $R_{No} = 4.5 \Omega$ .

Thus Norton's equivalent circuit is:-

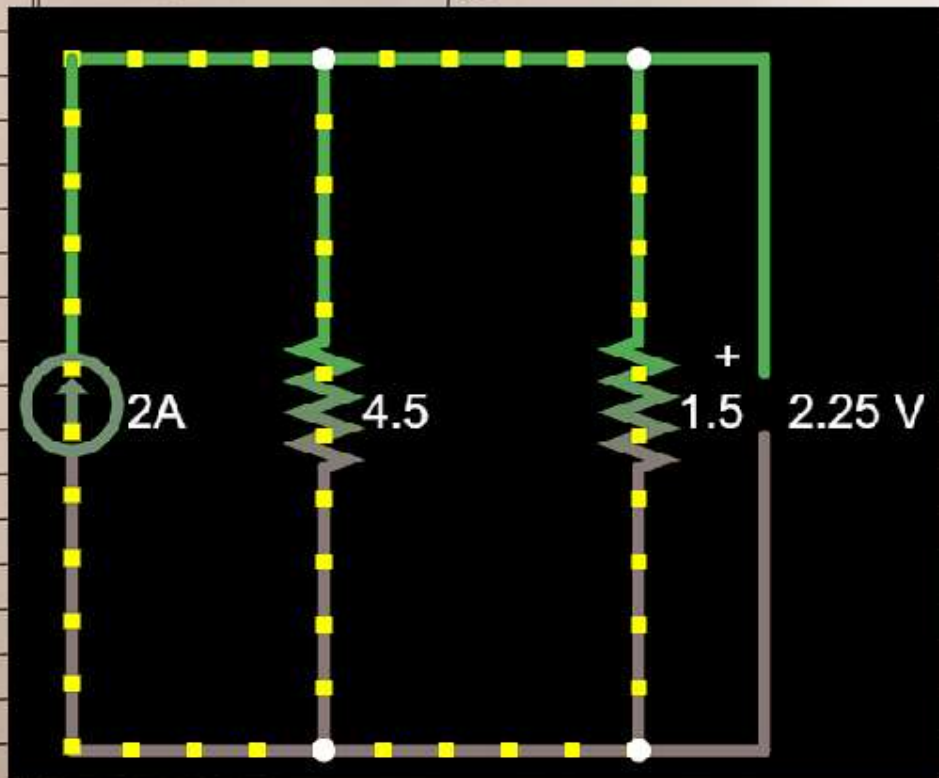

Teacher's Sign. : \_\_\_\_\_

EXPERIMENT:

No.

6

Verification of Norton's

Theorem using (dependent sources)

Page No.

Date

Using Norton's theorem find Norton's equivalent circuit about a-b.

→ To find  $V_{oc}$  ( $V_{AB}$ )

applying KCL at node Z

$$2i_x + i_x = i_1 - 8$$

$$3i_x - i_1 = -8 \quad \text{--- (1)}$$


KVL in loop A-Z-B-C-A

$$5i_x + 1i_1 = 40$$

$$5i_x + i_1 = 40 \quad \text{--- (2)}$$

On solving both equations, we get  
 $i_x = 4A$  &  $i_1 = 20A$
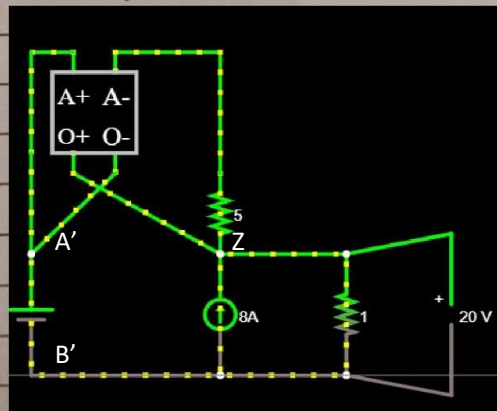
$$V_A = V_{AB} = 1 \times i_1 = 1 \times 20 = 20V$$





EXPERIMENT :

No.

Page No.

Date

Finding  $i_n$  short the open terminal.

Applying KVL

$$-40 + 5i_n = 0$$

$$i_n = 8$$


We can remove  $1\Omega$  resistance as it is shorted.

KCL at Z

$$3i_n = -8 + i_{Th}$$

$$i_{Th} = 32A$$
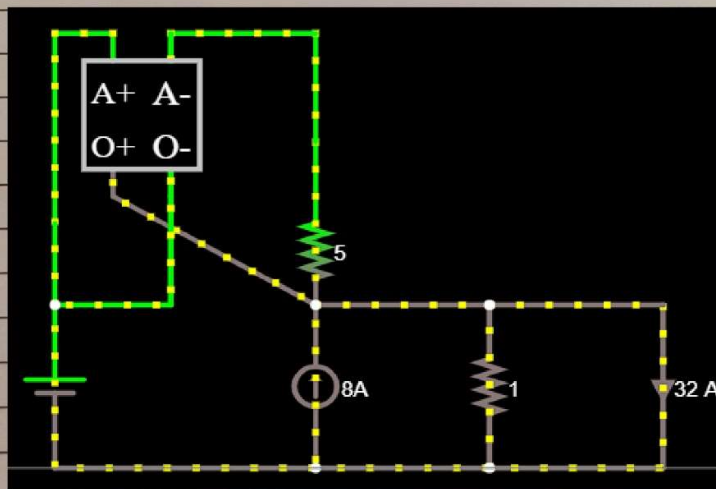
$$R_{Th} = \frac{V_{oc}}{I_{Th}} = \frac{20}{32} = 0.625\Omega$$



Teacher's Sign. :

# NORTON'S EQUIVALENT CIRCUIT

