

EXPERIMENT:

No. 8

Verification of Principle of
Maximum Power Transfer.

Page No.

20

Date

For the given circuit we need to compute R_L and find that the value at which maximum power is transferred by the source

→ We need to short the 8Ω

→ We need to short the $87V$ source

$$R_L = \frac{2 \times \left(\frac{8 \times 6}{14} + 1 \right)}{2 + \frac{8 \times 6}{14} + 1}$$

$$= \frac{2 \times 4.42}{8.42}$$

$$= \frac{8.84}{8.42}$$


$$R_L = 1.05 \Omega$$

For Maximum Power Transfer

$$R_L = R_{TH}$$

∴ Plotting R v/s P graph

| R | P (mW) |
|-----|--------|
| 0.7 | 1.218 |
| 1.4 | 1.375 |
| 2.1 | 1.325 |
| 2.8 | 1.215 |
| 3.5 | 1.116 |

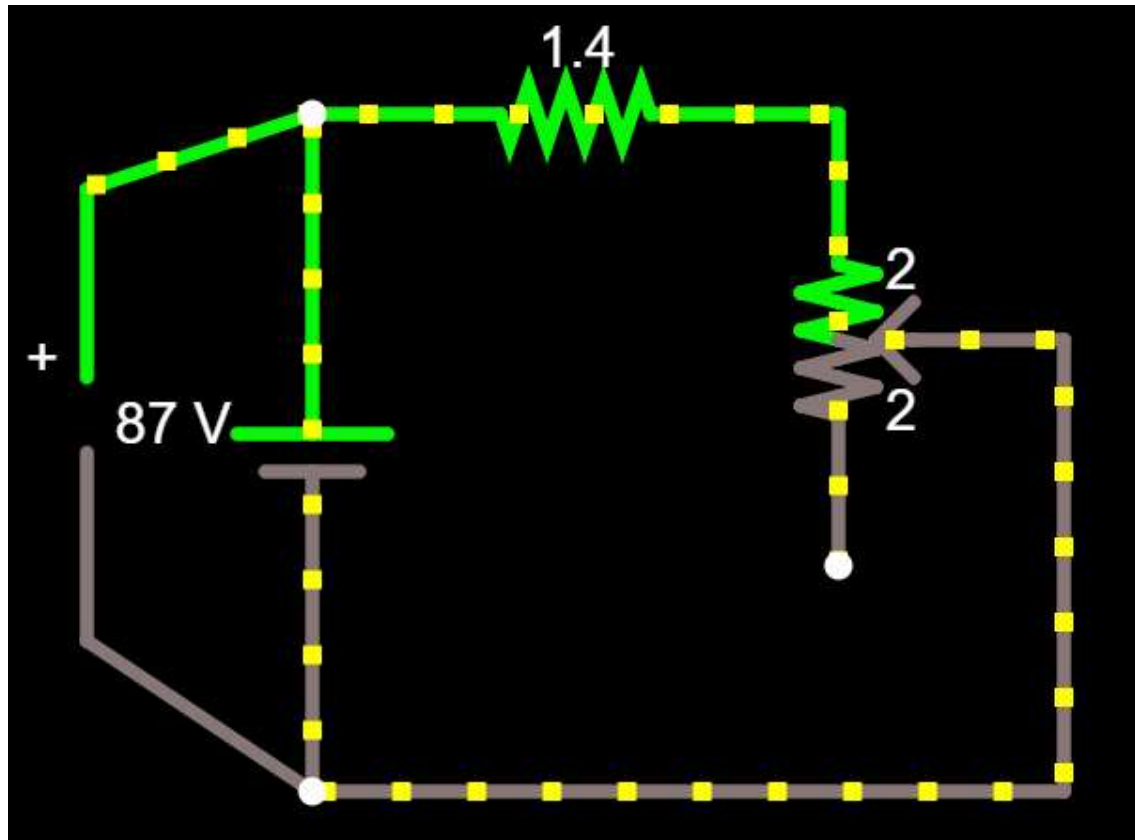

| R | N^P |
|-----|-------|
| 0.7 | 1.218 |
| 1.4 | 1.375 |
| 2.1 | 1.325 |
| 2.8 | 1.215 |
| 3.5 | 1.116 |

