

EXPERIMENT:

No.

2

Verification of KCL

Page No.

Date

20

11

21


KCL \rightarrow Kirchhoff's current Law

Q) Verify KCL by applying it in the circuit.

\rightarrow To find: Rate of current flowing through 2- Ω and 4- Ω resistors.

$$\leftarrow \text{KCL} \rightarrow$$
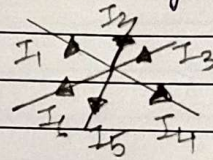
$$\sum I_{\text{incoming}} = \sum I_{\text{outgoing}}$$



$$I_1 + I_2 + I_3 = I_4 + I_5 + I_6$$

Points A, B, C, D, E form a node

$$\therefore I_2 + I_4 + 8 + 5 = 16 \quad (\text{KCL})$$

$$I_2 + I_4 = 16 - 13$$

$$I_2 + I_4 = 3 \text{ A} \quad \text{--- (1)}$$

Apply current division to find I_2

$$I_2 = \frac{I_1 \times 4}{2 + 4} = \frac{3 \times 4}{6} = 2 \text{ A}$$

$$\boxed{I_2 = 2 \text{ A}}$$

Recall equation (1)

$$\therefore I_4 = 3 - 2 = \underline{1 \text{ A}}$$

In the simulation we can see that the value of current matches with the above theoretical analysis. Thus, KCL is verified.

