


EXPERIMENT:

No. 6(a) Verification of Thevenin's Theorem

Page No.	
Date	

Q.7 Find load resistance across 5- Ω resistor, hence find thevenin equivalent circuit.

→ Circuit:-

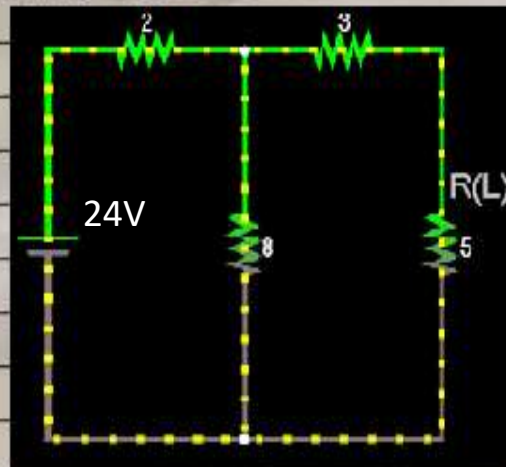

→ First remove 5- Ω from the circuit and short the voltage source to find out the R_{net} or R_{TH} .



$$R_{TH} = 3 + \frac{2 \times 8}{10}$$

$$= \cancel{4.4} \quad 4.6 \Omega$$

→ Now shorting 5- Ω and 8- Ω as shown in fig(2)

→ Now for V_{TH} , we remove the short and put back the 24V supply. Now, since 3- Ω is open no current passes through it.

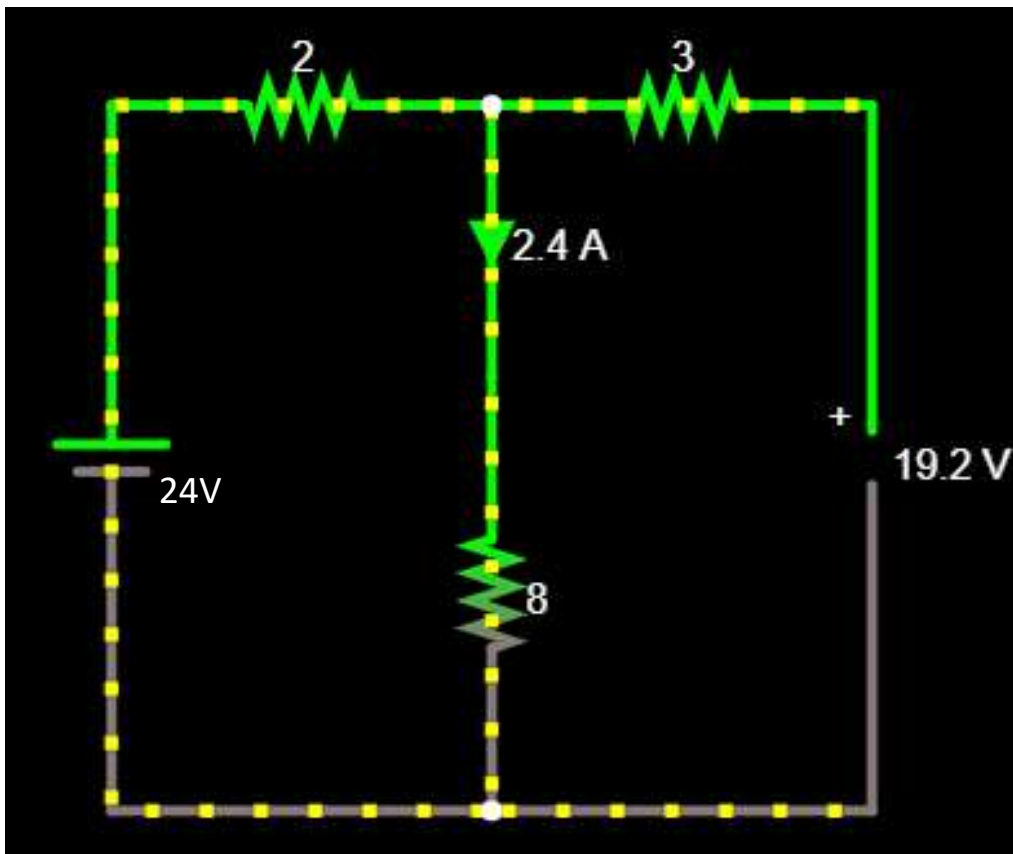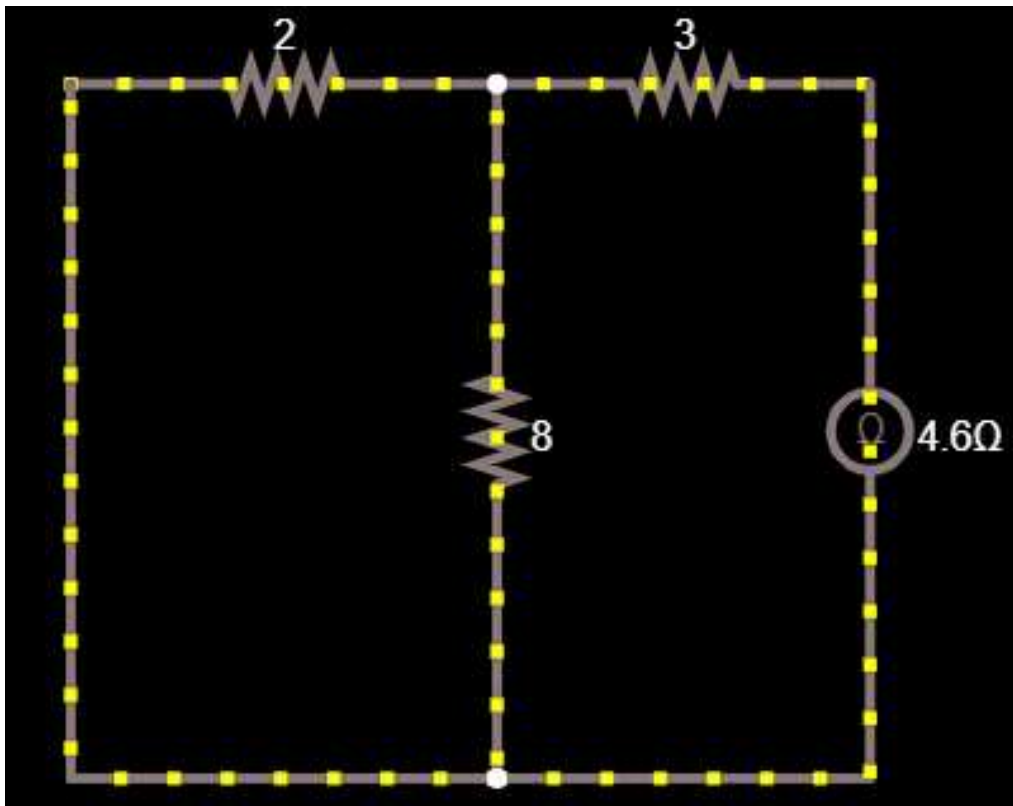→ Thus we'll find voltage difference across 8- Ω resistor.




Assume current (I) through the circuit (mesh say)

$$\therefore I = \frac{24}{10} = 2.4 \text{ A}$$

$$\therefore V_{Th} = V_8 = I \times 8 = 2.4 \times 8 = \underline{19.2V}$$

Thus we see thevenin ^{voltage} ~~current~~ is $19.2V$ and
resistance is 4.6Ω

Thevenin equivalent circuit:-

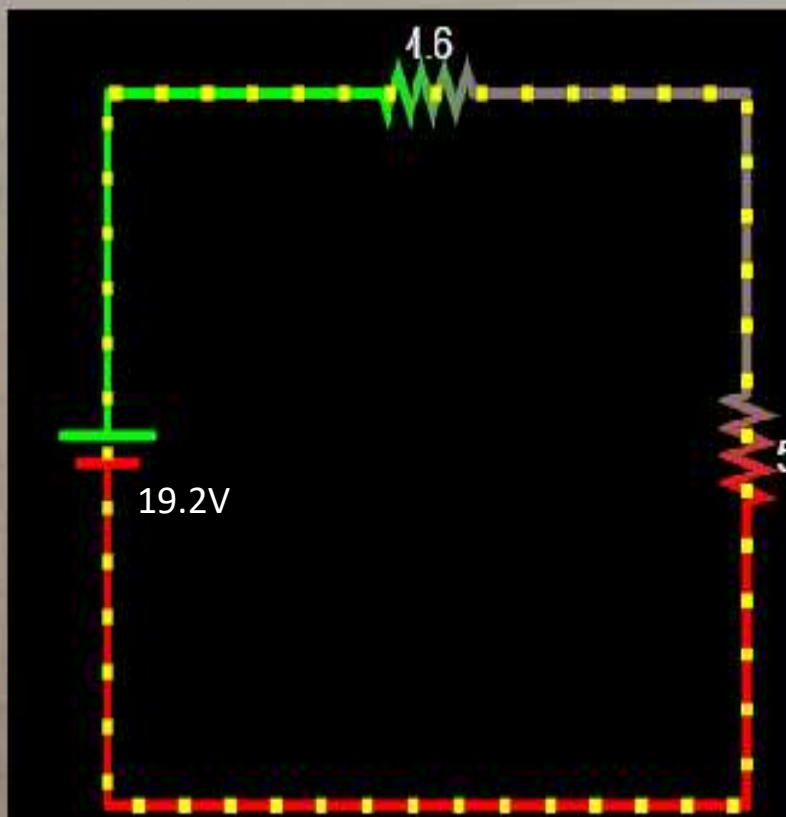

EXPERIMENT:


No.

Page No.

Date

$$I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{19.2}{5 + 4.6} = \frac{19.2}{9.6} = 2A$$

Thus Thevenins theorem is verified.

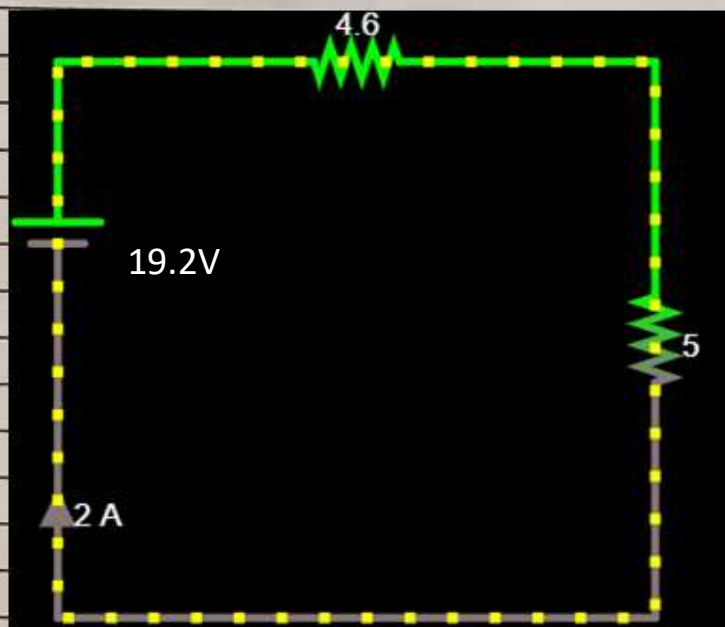

EXPERIMENT:

No. 66

Verification of
Thevenin's Theorem

Page No.

Date

Thevenin problem using dependent source.

→ Find the thevenin equivalent of the following circuit about a-b.

assume a current I .applying KVL to find V_o

$$V_{10K} + V_{20K} + 4V_o = 70$$

$$10K(I) + 20K(I) + 4V_o = 70$$

$$10K(I) + 20K(I) + 4(10K(I)) = 70$$

$$I(70K) = 70$$

$$I = \frac{1}{1000} \text{ A.}$$

$$I = 10^{-3} \text{ A}$$

$$\therefore V_o = 10^{-3} \times 10 \times 10^3$$

$$V_o = 10 \text{ V}$$

$$V_{ab} = 70V - V_o$$

$$= 70V - 10V$$

$$V_{ab} = 60V.$$



Thus, Thevenin equivalent voltage is 60V

Shorting all the voltage source and finding $R_{net}(R_{Th})$

$$R_{Th} = \left(\frac{1}{20K} + \frac{1}{10K} \right)^{-1}$$

$$= \frac{200K}{30} = 6.67K$$

Teacher's Sign. :

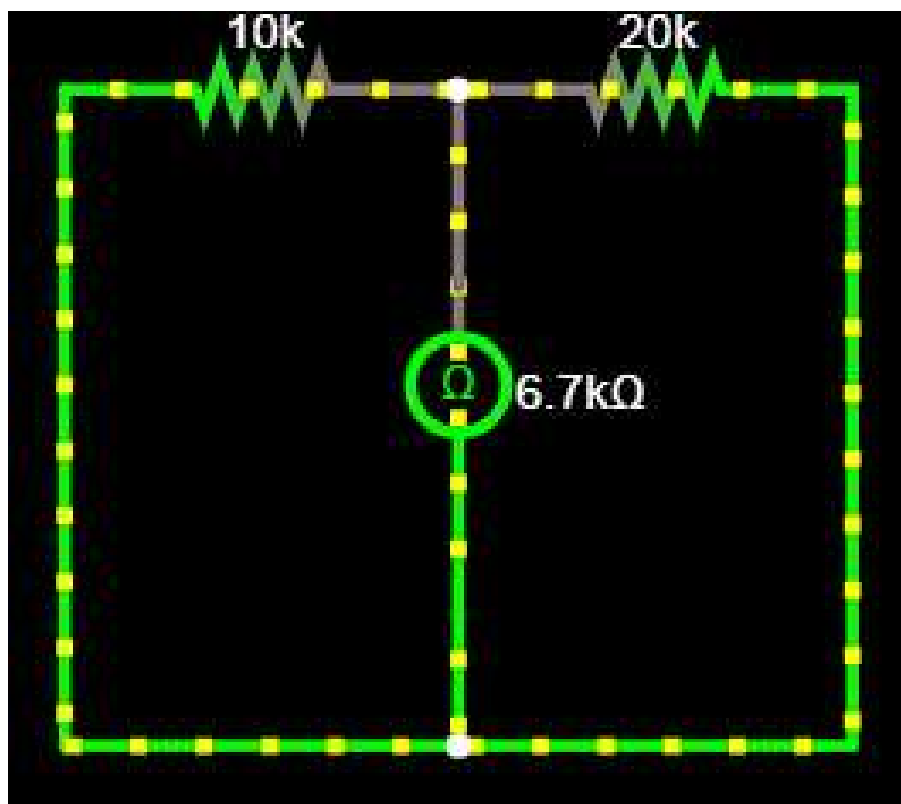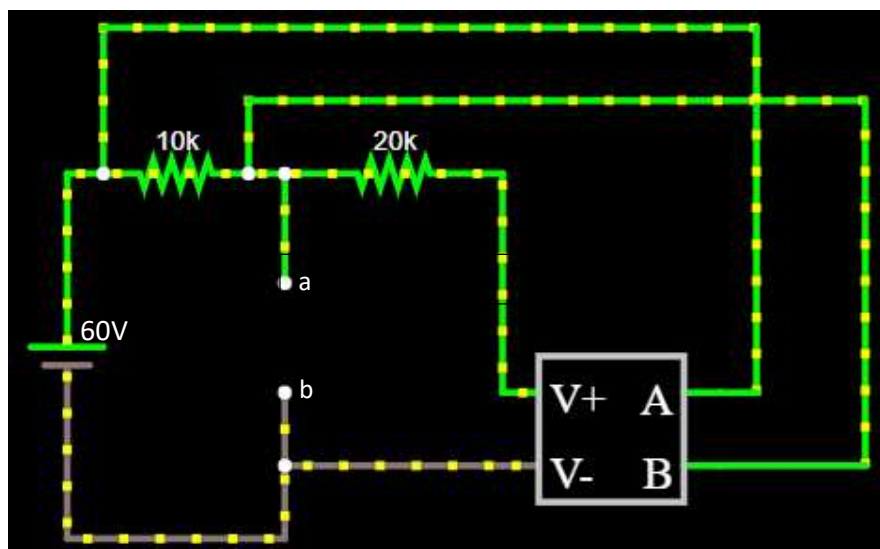

Thus, Thevenins, resistance is $6.67\text{K}\Omega$

$$I_{th} = \frac{V_{th}}{R_{th}} = \frac{60}{6.67\text{K}} = \underline{9\text{mA}}$$

$$\therefore I_{th} = 9\text{mA}$$

Thus, Thevenins theorem is verified

